


Theory of Computer Sciece: Homework #4 -
NandToTetris — Memory

Jeffrey Meyer Bayli Boston


November 15, 2018

1 Project 3


a) Bit All test passed

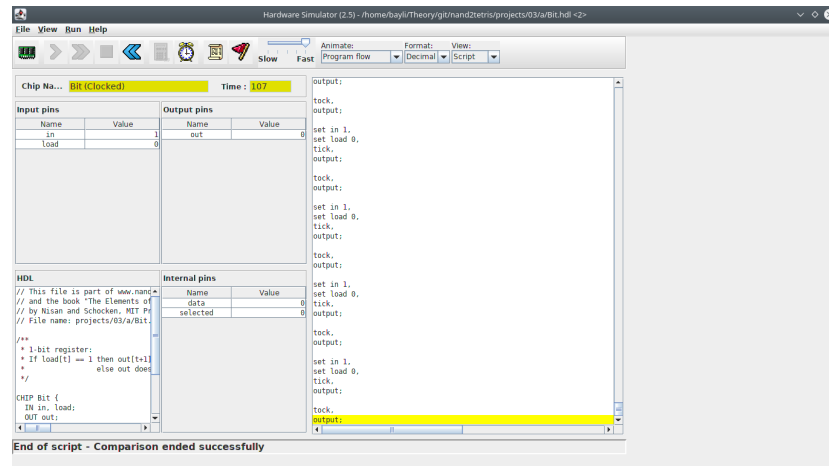


Register All test passed

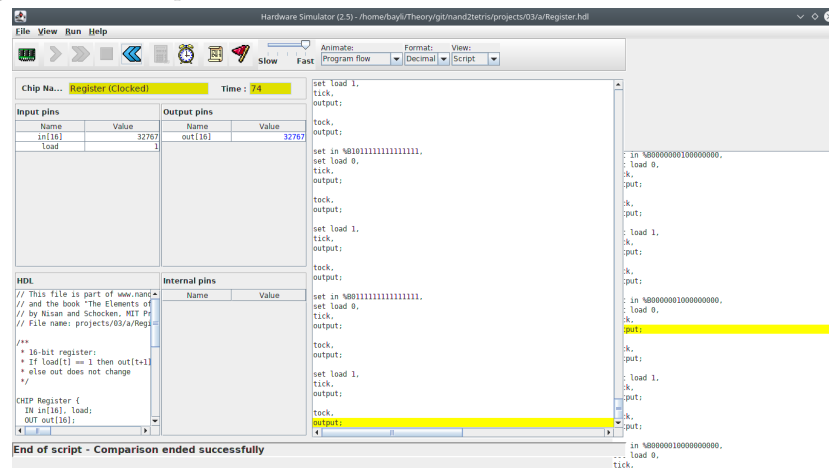


RAM8 All test passed

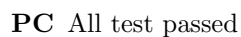


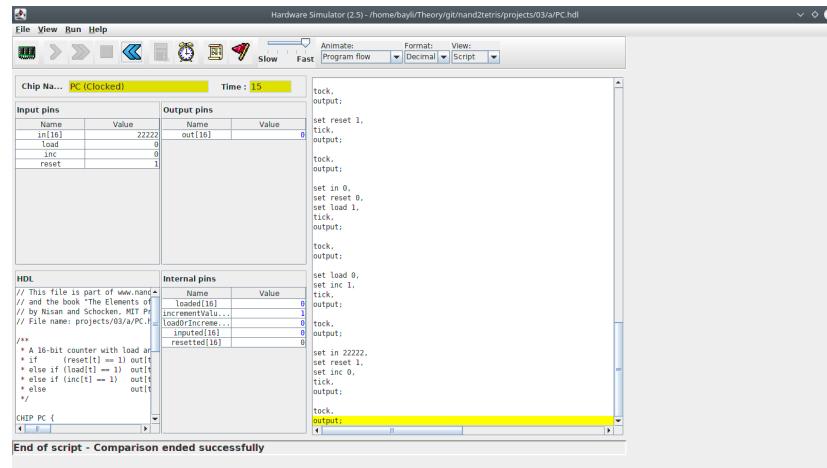


b) **RAM512** All test passed

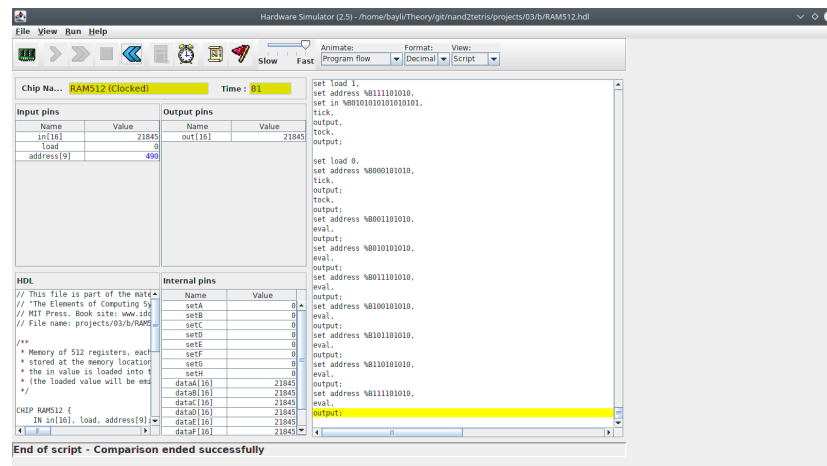

RAM4K All test passed

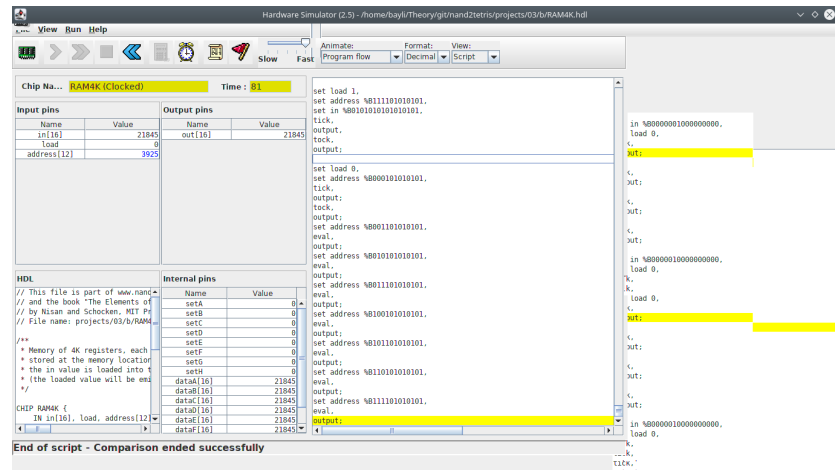

RAM16K All test passed

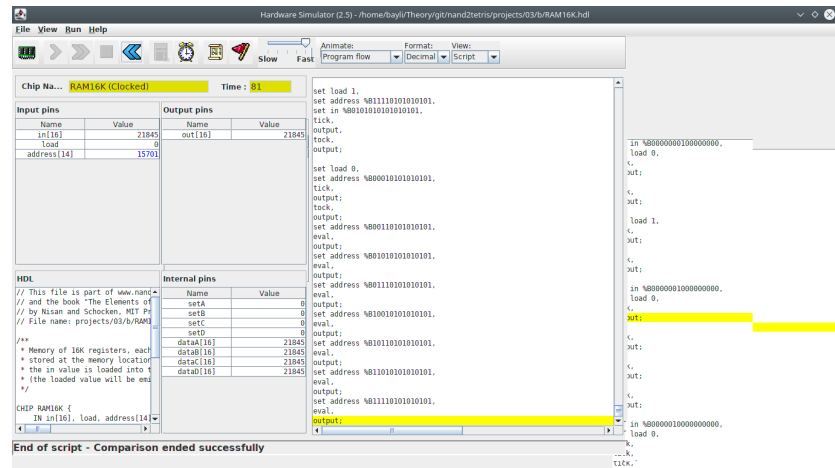

All documenting of whether a test file is adequate is at the top of each .tst file